

B. INS. & ELEC. ENGINEERING 2ND YEAR 1ST SEMESTER EXAMINATION 2025

ELECTRONIC CIRCUITS

TIME: 3 HOURS

FULL MARKS: 100

List of Course Outcomes (CO):

CO1: Classify and analyze different types of diode circuits (K2, K4, A1)

CO2: Identify and interpret the importance of biasing in electronic amplifiers (K3, A1)

CO3: Describe and explain the behavior of small signal amplifiers (K2, A1)

CO4: Differentiate and examine feedback circuits of various kinds (K4, A2)

CO5: Explain and analyze the operation of oscillators (K2, K4, A1)


Instructions to the Examinees:

- Each module in the question paper matches up with the corresponding CO
 - Attempt **ALL** the questions from **ALL** the modules for the attainment of all the Cos
 - Alternative questions (if any) exist within a module, not across the modules
-

[Turn over

MODULE 1ATTEMPT **ANY TWO** QUESTIONS FROM THIS MODULE

1. Show the voltage waveform across each half of the secondary winding and across the load resistor when a 100 V peak sine wave is applied to the primary winding in Fig. 1. What minimum PIV rating must the diodes have?

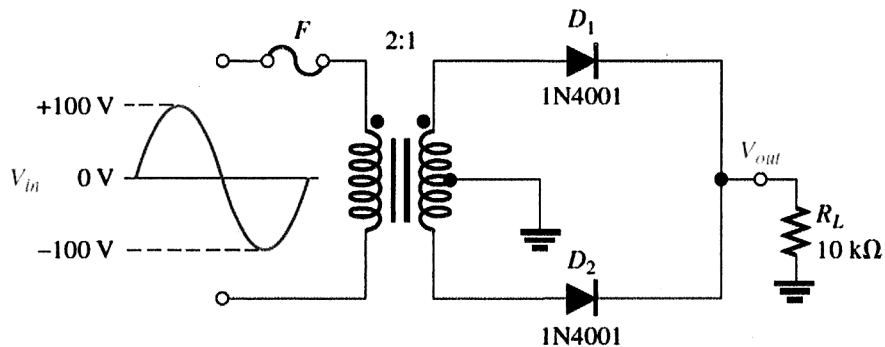
**Fig. 1**

6+4

- 2.
- (a) Draw and explain the operation of a positive clipper circuit. Draw the transfer characteristics of such a circuit when constructed using practical diode with a cut-in voltage of 0.65 V.
- (b) Show the effect of capacitor in eliminating the ripple content from a rectified output voltage.

(3+2)+5

3. For the circuit in Fig. 2, determine the output voltage at minimum and maximum zener current. Calculate the value of R that should be used. What is the minimum value of R_L that can be used? Given $V_Z = 15\text{ V}$ @ $I_Z = 17\text{ mA}$, $I_{ZK} = 0.25\text{ mA}$, $Z_Z = 14\ \Omega$ and $P_{\max} = 1\text{ W}$.

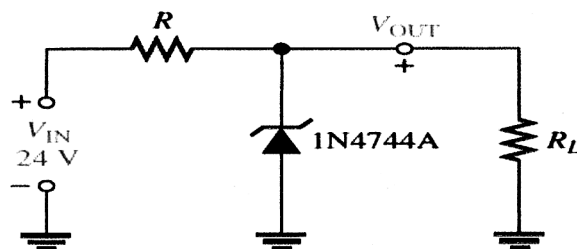
**Fig. 2**

5+5

MODULE 2**ATTEMPT ANY TWO PARTS FROM Q. No. 4**

4.

- (a) Find out the expression for quiescent collector current for a collector-feedback bias circuit.
- (b) Determine whether or not the transistor shown in Fig. 3 is in saturation. Assume $V_{CE(sat)} = 0.1 \text{ V}$.

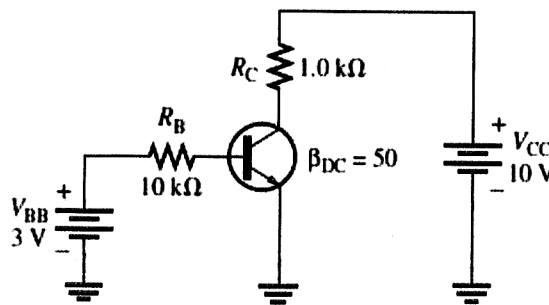**Fig. 3**

- (c) What is the significance of load line? How can the slope of the load line be adjusted?
- (d) Mention the basic difference between stiff and non-stiff voltage divider bias.

2X5

MODULE 3**ATTEMPT Q. NO. 5 AND ANY ONE FROM THE REST**

5. For the common emitter amplifier shown in Fig. 4, calculate (i) the mid-band gain (ii) 3-dB bandwidth using appropriate graph paper. The transistor's datasheet provides the following: $\beta_{ac} = \beta_{dc} = 80$, $V_A = \infty$, $c_\pi = 20 \text{ pF}$, $c_\mu = 2.4 \text{ pF}$. Consider appropriate number of frequency points both in the low and high frequency range in drawing the frequency response. Assume $V_T = 25 \text{ mV}$.

[Turn over

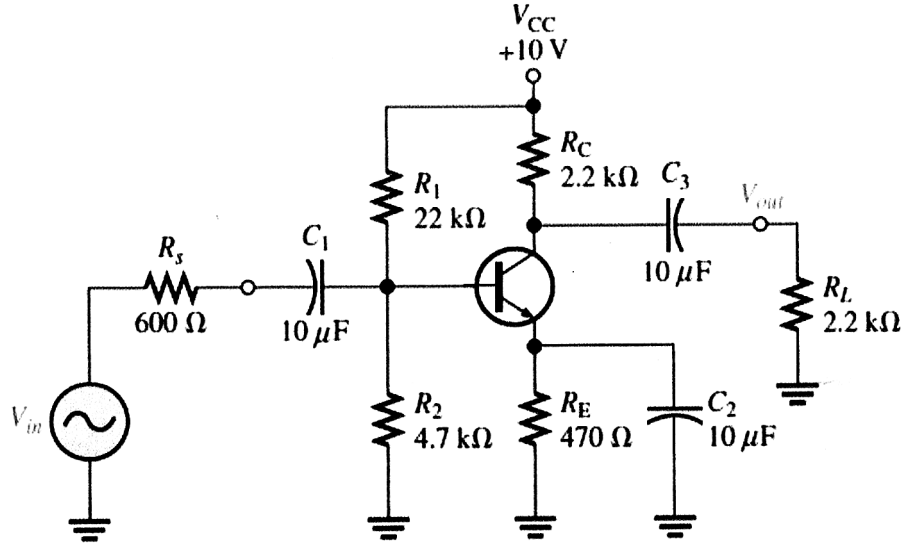


Fig. 4

10+30

6. Show that the small-signal voltage gain of a common-base amplifier is given by:

$$A_v = g_m \left(\frac{R_C \parallel R_L}{R_S} \right) \left[\left(\frac{r_\pi}{1 + \beta} \right) \parallel R_E \parallel R_S \right]$$

Where the symbols enjoy their usual significances.

10

7.

- (a) What do you understand by differential signal?
(b) Draw and explain the large signal characteristics of a differential amplifier circuit.

2+8

MODULE 4

8. Draw the diagram of a two-stage common emitter amplifier circuit which exhibits current-shunt feedback. Hence calculate the expression of feedback factor and current gain with feedback.

10

MODULE 5

9. Draw the diagram of an RC phase-shift oscillator circuit. Calculate its oscillation frequency.

10

-----X-----