

(6)

[CO5 : Microprocessor]

9. (a) Write names and sizes of user accessible registers of 8085 μ P. What are the functions of flag register?
(b) Explain what happens on execution of the instructions MOV B, C and MOV D, M. 4+4
10. (a) What are the essential connections of a memory chip?
(b) Draw a schematic diagram of memory chip connection with μ P and explain what signals μ P generate to read a data byte from memory. 3+5

★ ★ ★

Ex/SC/PHY/UG/CORE/TH/07/2024

B. Sc. EXAMINATION, 2024

(2nd Year, 1st Semester)

PHYSICS (HONOURS)

PAPER – CORE 7

(Digital Systems and Applications)

Time : Two Hours

Full Marks : 40

Answer any *one* question from each CO


[CO1 : Number system & Logic Gates]

1. (a) Convert decimal number $12\frac{3}{32}$ to binary. [Hint : Express the number in hexadecimal, taking the denominator of the fractional part of the number in power of 16]
- (b) Consider the $(123)_5 = (X8)_Y$ is a correct equation where X and Y are unknown. Find the possible solutions for X and Y and show that number at RHS of equation may be a decimal number.
- (c) Subtract the hexadecimal number 4A0E.A9 from 67F2.6E using 2's complement arithmetic and represent the results in sign magnitude binary number format.
- (d) Draw the circuit diagram of 2-input NOR gate.


2+2+2+2

(2)

 2. (a) Add the hexadecimal numbers 4A0E.A9 and 67F2.6E. Write down the result in binary format.
- (b) Show that the circuit given below represent basic logic gate if $C = 0$.



 - (c) In the circuit shown in figure below, the output is required to be $Y = AB + \bar{C}\bar{D}$. What are the gates G1 and G2 must be?



(5)

 
- (b) Draw a logic circuit using SR flip-flop (FF) where $S = J\bar{Q}_n$ and $R = KQ_n$, J and K are two external input. Write down the characteristic table of the circuit and show that it will act as a JK FF. 5+3

[CO4 : Sequential logic circuit]

7. (a) Draw circuit diagram of a 3 bit ripple counter using negative edge triggered JK-flip-flop. Explain its count sequence for a complete count period and also show timing diagrams. What is the main disadvantage of a ripple counter?
- (b) Suppose by some connection error in the above circuit for the middle flip flop Q and Q' have been exchanged. Write out the count sequence for this circuit. 5+3
8. (a) Draw the circuit diagram of a Parallel In Serial Out (PISO) shift register and explain its operation.
- (b) A 4-bit shift register circuit is converted into a counter by connecting $\bar{Q}$ of last flip-flop to its input. Write its count sequence. 4+4

(3)

- (d) The output of the logic gate given in figure below is $F(A, B) = \overline{A}B$. Design a two input NAND gate using this gate.


$$2+2+2+2$$

[CO2 : Boolean algebra & Karnaugh map]

3. (a) Explain whether the NAND operation is commutative and associative or not. Design a 3 input NAND using 2 input NAND gates.

- (b) Reduce the Boolean expression $\overline{\overline{ABC(A+B)+BC}}$ in minimal form.

- (c) Implement the function

$$F(A,B,C,D)=\overline{A}\overline{B}\overline{C}+A\overline{B}D+\overline{A}\overline{B}C\overline{D}; d=ABC+A\overline{B}\overline{D}$$

using all NAND gates.

 $3+2+3$

4. (a) If the Boolean function $Z = PQ + PQR + PQRS + PQRST + PQRSTU$, then find $\bar{Z}$ in minimal form.

- (b) The four variable function F is given as :
 $F(A, B, C, D) = \sum m(2, 3, 8, 10, 11, 12, 14, 15)$. Reduce
 F in SOP, POS, NAND and NOR formats and realize it
 using NOR gates. 2+6

2+6


PHY-331

[Turn Over]


(4)

[CO3 : Combinational logic circuit & flip flop]

 5. (a) Show that in circuit given below the LED should not glow irrespective of switch position.



 - (b) Find the required input conditions (A, B, C) for which the output of the logic circuit shown in figure below will be $Z = 1$.



6. (a) What is multiplexer (MUX)? Write down the job supposed to be executed by a 4 to 1 line MUX and hence obtain the truth table and determine the logic expression for its outputs. Draw its circuit diagram.

PHY-331

[Continued]